The City School, PAF Chapter

Junior A Section

Science Reinforcement Worksheet-1

Jr.IV

Q1: Give reasons:	
a) A circuit works when	
b) We should not fly kites near electric wires because	
c) Power lines are more dangerous than electricity mains because	
Q2: Fill in blanks:	
a) The electricity in a circuit has to flow through all the	_ in
the circuit.	
b) The more batteries you use, the the motor will turn.	
c) Metals electricity.	
d) 'V' stands for	
e) are used to join parts of a circuit.	
Q3. Give one word answer.	
a) Something that does not allow heat to go through it	
b) Something which can make a gap in a circuit, to turn other things on or	
off	
c) Part of a plug that conducts electricity	
d) A short way of saying electricity mains	
e) Something that makes a noise when electricity flows through it	

The City School, PAF Chapter

Junior A Section

Science Reinforcement Worksheet-1

Jr.IV

d) A circuit works when e) We should not fly kites near electric wires because f) Power lines are more dangerous than electricity mains because Q2: Fill in blanks: f) The electricity in a circuit has to flow through all thein the circuit. g) The more batteries you use, the the motor will turn. h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	Q1: 0	Give reasons:
f) Power lines are more dangerous than electricity mains because Q2: Fill in blanks: f) The electricity in a circuit has to flow through all the	d)	A circuit works when
Q2: Fill in blanks: f) The electricity in a circuit has to flow through all the in the circuit. g) The more batteries you use, the the motor will turn. h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	e)	We should not fly kites near electric wires because
f) The electricity in a circuit has to flow through all thein the circuit. g) The more batteries you use, the the motor will turn. h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	f)	Power lines are more dangerous than electricity mains because
the circuit. g) The more batteries you use, the the motor will turn. h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	Q2: F	ill in blanks:
g) The more batteries you use, the the motor will turn. h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	f)	The electricity in a circuit has to flow through all the ir
h) Metals electricity. i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or		the circuit.
 i) 'V' stands for j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or 	g)	The more batteries you use, the the motor will turn.
 j) are used to join parts of a circuit. Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or 	h)	Metals electricity.
Q3. Give one word answer. f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	i)	'V' stands for
f) Something that does not allow heat to go through it g) Something which can make a gap in a circuit, to turn other things on or	j)	are used to join parts of a circuit.
g) Something which can make a gap in a circuit, to turn other things on or	Q3. 0	Give one word answer.
	f)	Something that does not allow heat to go through it
OII	g)	
h) Part of a plug that conducts electricity	h)	
i) A short way of saying electricity mains		
j) Something that makes a noise when electricity flows through it	۱)	